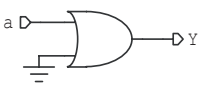
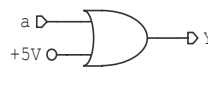
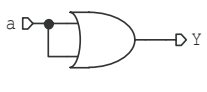
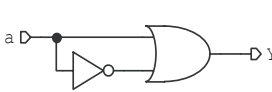
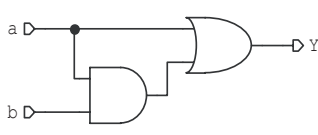
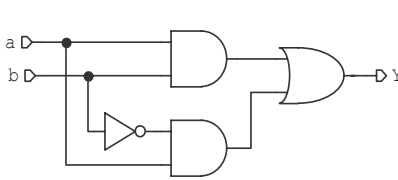
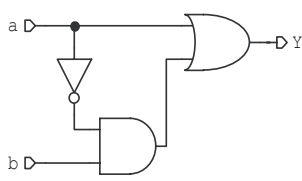
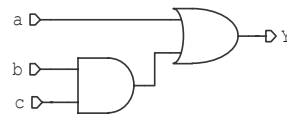


Aula 3

Teoremas Booleanos .

Obs.: Para essa prática você deverá identificar os componentes/pinos utilizados (datasheet).

T1. Analisar os circuitos abaixo, preencher a tabela verdade e verificar através de montagem.

$A + 0 = A$  <table border="1"> <thead> <tr> <th>a</th> <th>a+0</th> </tr> </thead> <tbody> <tr> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td></td> </tr> </tbody> </table>	a	a+0	0		1		$A + 1 = 1$  <table border="1"> <thead> <tr> <th>A</th> <th>a+1</th> </tr> </thead> <tbody> <tr> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td></td> </tr> </tbody> </table>	A	a+1	0		1																																																	
a	a+0																																																												
0																																																													
1																																																													
A	a+1																																																												
0																																																													
1																																																													
$A + \bar{A} = 1$  <table border="1"> <thead> <tr> <th>a</th> <th>a+a</th> </tr> </thead> <tbody> <tr> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td></td> </tr> </tbody> </table>	a	a+a	0		1		$\bar{A} + A = 1$  <table border="1"> <thead> <tr> <th>a</th> <th>a+a</th> </tr> </thead> <tbody> <tr> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td></td> </tr> </tbody> </table>	a	a+a	0		1																																																	
a	a+a																																																												
0																																																													
1																																																													
a	a+a																																																												
0																																																													
1																																																													
$A + AB = A$  <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>a+ab</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>	a	b	a+ab	0	0		0	1		1	0		1	1		$AB + \bar{A}B = B$  <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>ab+a-barb</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>	a	b	ab+a-barb	0	0		0	1		1	0		1	1																															
a	b	a+ab																																																											
0	0																																																												
0	1																																																												
1	0																																																												
1	1																																																												
a	b	ab+a-barb																																																											
0	0																																																												
0	1																																																												
1	0																																																												
1	1																																																												
$A + \bar{A}B = A + B$  <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>a+a-barb</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td></td> </tr> <tr> <td>1</td> <td>1</td> <td></td> </tr> </tbody> </table>	a	b	a+a-barb	0	0		0	1		1	0		1	1		$A + BC = (A + B)(A + C)$  <table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>c</th> <th>a+bc</th> <th>(a+b)(a+c)</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table>	a	b	c	a+bc	(a+b)(a+c)	0	0	0			0	0	1			0	1	0			0	1	1			1	0	0			1	0	1			1	1	0			1	1	1		
a	b	a+a-barb																																																											
0	0																																																												
0	1																																																												
1	0																																																												
1	1																																																												
a	b	c	a+bc	(a+b)(a+c)																																																									
0	0	0																																																											
0	0	1																																																											
0	1	0																																																											
0	1	1																																																											
1	0	0																																																											
1	0	1																																																											
1	1	0																																																											
1	1	1																																																											

T2. Para os circuitos a seguir, você deverá efetuar as montagens no simulador digital_97


$AB + \bar{A}C = (A \cdot C) \cdot (\bar{A} \cdot B)$

a	b	c	$ab + \bar{a}c$	$(a \cdot c) \cdot (\bar{a} \cdot b)$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$AB + \bar{A}C + BC = AB \cdot \bar{A}C$

a	b	c	$ab + \bar{a}c + bc$	$ab \cdot \bar{a}c$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 - T3. Projetar um circuito com duas entradas (habilita e dado) e uma única saída “S” de tal forma que quando habilita = 0, S = 0 e quando habilita = 1, S = dado. Montar o circuito e verificar seu funcionamento; Conectar a entrada “dado” a um sinal de frequência conhecida e verificar o comportamento da saída “S” em função da entrada habilita.



- T4. Repetir o item anterior utilizando portas NAND.

Relatório:

Para a parte T1 apresentar uma foto das montagens, a equação e a tabela verdade de cada caso. Para as partes T2, T3 e T4 apresentar um printscreen do simulador, as equações e tabela verdade de cada exercício.

DM74LS32

Quad 2-Input OR Gate

General Description


This device contains four independent gates each of which performs the logic OR function.

Ordering Code:

Order Number	Package Number	Package Description
DM74LS32M	M14A	14-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-120, 0.150 Narrow
DM74LS32SJ	M14D	14-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide
DM74LS32N	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

Connection Diagram

 

Function Table

$$Y = A + B$$

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H

H = HIGH Logic Level
L = LOW Logic Level

DM7408 Quad 2-Input AND Gates


General Description

This device contains four independent gates each of which performs the logic AND function.

Features

- Alternate Military/Aerospace device (5408) is available.
Contact a Fairchild Semiconductor Sales
Office/Distributor for specifications.

Connection Diagram

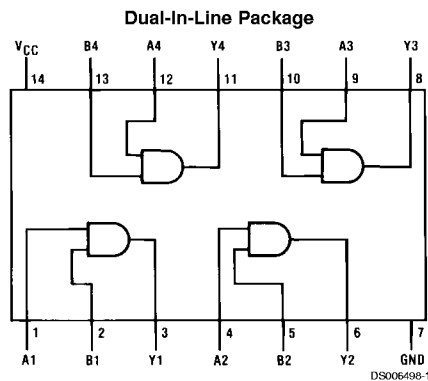

Order Number 5408DMQB, 5408FMQB, DM5408J, DM5408W or DM7408N
See Package Number J14A, N14A or W14B

Function Table

$$Y = AB$$

Inputs		Output
A	B	Y
L	L	L
L	H	L
H	L	L
H	H	H

H = High Logic Level
L = Low Logic Level

DM74LS00

Quad 2-Input NAND Gate

General Description


This device contains four independent gates each of which performs the logic NAND function.

Ordering Code:

Order Number	Package Number	Package Description
DM74LS00M	M14A	14-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-120, 0.150 Narrow
DM74LS00SJ	M14D	14-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide
DM74LS00N	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

Connection Diagram

 

Function Table

$$Y = \overline{AB}$$

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

H = HIGH Logic Level
L = LOW Logic Level